



Cairo University Faculty of Engineering  
Computer Engineering Department  
CMPN202



# **PHYN212**

## **Electromagnetics for Computer Engineers**

### **Project**

Name: Marly Mofeed Makram


Code: 1200909

## Analytic formula & Result values:

Masly Mofeed Makram

1200909

Project 1 EM

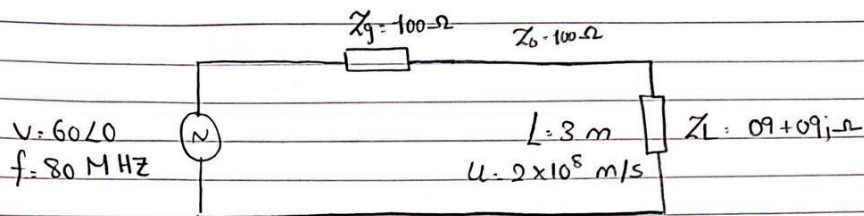

$$1) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{9 + 9j - 100}{9 + 9j + 100} = 0.83609 \angle 169.6316^\circ$$

$$\approx \frac{-4919}{5981} + \frac{900}{5981}j = 0.83609 \angle 2.96063 \text{ radians}$$

$$2) VSWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.83609}{1 - 0.83609} = 11.20181$$

$$3) Z_{in}(v) = Z_0 \frac{Z_L + jZ_0 \tan(\beta L)}{Z_0 + jZ_L \tan(\beta L)}$$

$$\text{to get } \beta = \frac{\omega}{v} = \frac{2\pi \times 80 \times 10^6}{2 \times 10^8} = 0.8\pi = 1.414^\circ \quad \beta L = 1.414 \times 3 = 4.32$$

$$4.32 - 360 = -72^\circ$$

$$Z_{in}(v) = 100 \times \frac{(9 + 9j) + j \times 100 \times \tan(0.8\pi \times 3)}{100 + j(9 + 9j) \tan(0.8\pi \times 3)} \rightarrow \text{radians}$$

$$900 + 31676.83537j$$

$$72.30084817 + 27.69915183j$$

$$= 409.2935 \angle 1.17653 \rightarrow \text{radians}$$

$$= 409.2935 \angle 67.41 \rightarrow \text{Degrees}$$


4)

$$I_{SC} = \frac{V_g}{Z_g + Z_{in}}$$

$$= \frac{60}{100 + 409.2935 \angle 67.41^\circ}$$

$$= 0.131254 \angle -55.7576^\circ \rightarrow \text{degrees}$$
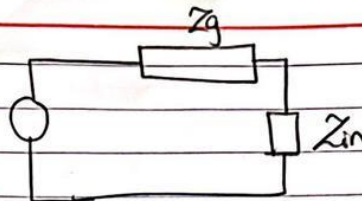
$$= 0.131254 \angle -0.97315 \rightarrow \text{radians}$$



$$5) P_{avg} = \frac{1}{2} \operatorname{Re} [V_{SC} \times I_{SC}^*]$$

$$V_{SC} = \frac{V_g}{Z_g + Z_{in}} = I_{SC} \times Z_{in}$$

$$= 53.7214 \angle 11.6524^\circ \rightarrow \text{degrees}$$

$$= 53.7214 \angle 0.20337 \rightarrow \text{Radians}$$

$$P_{avg} = \frac{1}{2} \operatorname{Re} [53.7214 \angle 11.6524^\circ \times 0.131254 \angle -55.7576^\circ]$$

$$P_{avg} = \frac{1}{2} \operatorname{Re} [2.70858 + 6.510j]$$

$$\frac{1}{2} [2.70858] = 1.35429 \text{ Watt}$$

$$6) P_{avg} = \frac{1}{2} \frac{|V_o|^2}{Z_o} [1 - |\Gamma|^2]$$

$$1.35429 = \frac{1}{2} \frac{|V_o|^2}{100} [1 - (0.83609)^2]$$

$$|V_o| = 29.99 \approx 30$$

$$V_{max} = |V_o| [1 + |\Gamma|] = 30 [1 + 0.83609] = 55.0827$$

$$V_{min} = |V_o| [1 - |\Gamma|] = 30 [1 - 0.83609] = 4.9173$$

$$I_{max} = \frac{V_{max}}{Z_o} = \frac{55.0827}{100} = 0.550827 \text{ A}$$

$$I_{min} = \frac{V_{min}}{Z_o} = \frac{4.9173}{100} = 0.049173 \text{ A}$$

$$Z_{inmax} = \frac{V_{max}}{I_{min}} = 1120.181807$$

$$Z_{inmin} = \frac{V_{min}}{I_{max}} = 8.92712$$



Scanned with CamScanner

$$7) |V_{cmax}| = V_0 + e^{-j\beta z} [1 + \Gamma_L e^{-j2\beta l}]$$

$$55 - 0.827 = 30 e^{-j0.8\pi z} [1 + 0.83609 \angle 169.6316 \times e^{-j2 \times 0.8\pi (3-z)}]$$

$$Z = 0.10463966 + 0.1473467i = 0.18071729 \angle 54.618 \rightarrow \text{degrees}$$

$$8) V_s(z) = V_0 + e^{-j\beta z} [1 + \Gamma_L e^{-j2\beta l}] \quad l = 1 - z$$

$$= 30 e^{-j \times 0.8\pi z} [1 + (0.83609 \angle 169.6316) e^{-j2 \times 0.8\pi (1-z)}]$$

$$9) I_s(z) = \frac{30}{100} e^{-j \times 0.8\pi z} [1 - (0.83609 \angle 169.6316) e^{-j2 \times 0.8\pi (1-z)}]$$

$$10) Z_{in}(z) = 100 \times \frac{9 + 9j + j \times 100 \tan(0.8\pi(3-z))}{100 + j(9 + 9j) \tan(0.8\pi(3-z))}$$

$$100 + j(9 + 9j) \tan(0.8\pi(3-z))$$

$$\text{from } Z_0 \frac{Z_L + j Z_0 \tan \beta(l-z)}{Z_0 + j Z_L \tan \beta(l-z)}$$



Scanned with CamScanner

```
3;
% Vs(z) according to the equation
% exp(-0.8j*pi*z) .* (1 + 0.83609 .* exp(2.960629j*pi) .* exp(-1.6j*pi*(3-z)));
Vs(Vs));
Vs(Vs));
[Index]=max(abs(Vs));
Index);
```

	1	2	3	4	5
1	2.4000				
2					
3					
4					
5					
6					
7					
8					
9					
10					
11					
12					

```

1 syms z
2
3 vs = 30 * exp(-1i * 0.8 * pi * z) * (1 + (-0.82243738 + 0.15047668i) * exp(-2i * 0.8 * pi * (3 - z)));
4 abs_vs = abs(vs);
5
6 figure(1);
7 fplot(abs_vs, [0, 3]);
8 title('Absolute value of voltage along transmission line');
9 xlabel('z');
10 ylabel('|vs|');
11
12 Is = (30/100)*exp(-1i * 0.8 * pi * z) * (1 + (-0.82243738 + 0.15047668i) * exp(-2i * 0.8 * pi * (3 - z)));
13 abs_Is = abs(Is);
14
15 figure(2);
16 fplot(abs_Is, [0, 3]);
17 title('Absolute value of current along transmission line');
18 xlabel('z');
19 ylabel('|Is|');
20
21 zin = 100*((9+9i+100*tan(0.8*pi*(3-z)))/(100+1*(9+9i)*tan(0.8*pi*(3-z))));
22 abs_zin = abs(zin);
23
24 figure(3);
25 fplot(abs_zin, [0, 3]);
26 title('Magnitude of input impedance along transmission line');
27 xlabel('z');
28 ylabel('|Zin|');
29

```

